

# Unit-7

## Polyphase circuits

Prepared by:

Jigar Sarda


M & V Patel Department of Electrical Engineering

[jigarsarda.ee@charusat.ac.in](mailto:jigarsarda.ee@charusat.ac.in)



**CHARUSAT**  
CHAROTAR UNIVERSITY OF SCIENCE AND TECHNOLOGY

# Introduction

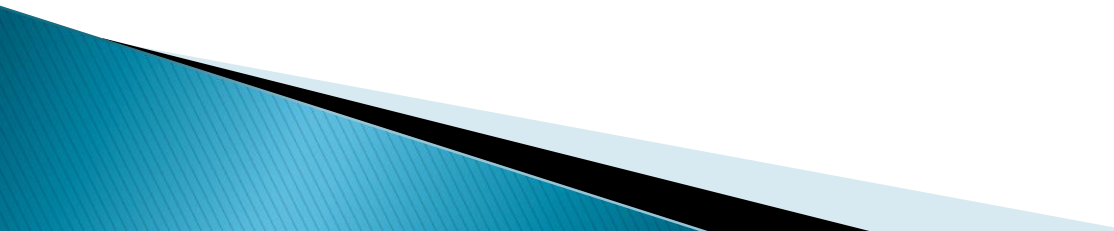- The generator producing a single-phase supply has only one armature winding.
  - But if the generator is arranged to have three separate but identical winding displaced 120 degree apart and rotate in a common magnetic field, it produces three voltages of same magnitude and frequency but displaced by 120 degree electrical from one another. This is called a three-phase system.
- 

# Advantages of 3-phase system over single-phase system <sup>3</sup>

1. **Constant Power:-** In a single phase system, output power varies sinusoidally at a frequency twice the supply frequency.
  - ▶ This pulsating nature of current is harmful to some applications whereas the balanced 3-phase system supplies constant current at all instants of time.
2. **Self start:-** The 3-phase systems are self starting as they do not require any starting device.
  - ▶ However, single phase systems require starting device.


# Advantages of 3-phase system over single-phase system <sup>4</sup>

3. **Greater output:-** The power generated by a 3-phase system is greater than that of a single phase system for a given volume and weight of the generator.
  - ▶ This is the distinct advantages over the single phase generator
4. **More economical:-** The 3-phase system is much smaller and less expensive than single phase system because less material is required for a given output power at a given voltage.


# Advantages of 3-phase system over single-phase system <sup>5</sup>

5. **Less voltage drop:-** The voltage drop from the generator to the load is less in a 3-phase system in comparison to the single-phase system
6. **Power transmission economics:-** The conductor material required to transmit a given power at a given voltage of material required in single phase system.
  - ▶ This means a saving in material and strength of transmitting towers.
7. **High Efficiency:-** The 3-phase motors are efficient and have a higher power factor than single phase motors of the same capacity.

# Phase sequence

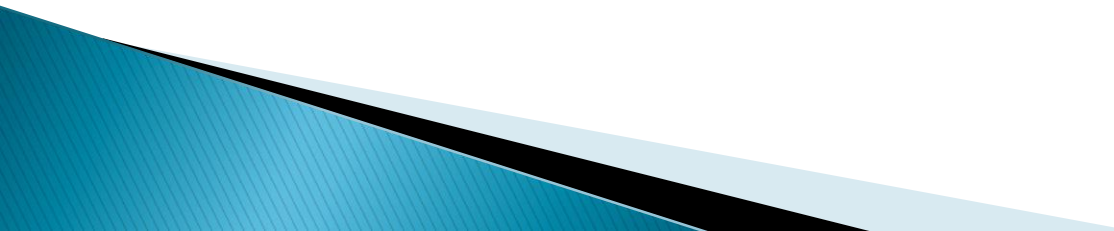- ▶ In three phase system, there are three voltages having same magnitude and frequency displaced by an electrical angle of 120 degree.
  - ▶ They are attaining their positive maximum value in a particular order.
  - ▶ The order in which voltages in the three-phase attain their maximum positive value is known as phase sequence.
- 
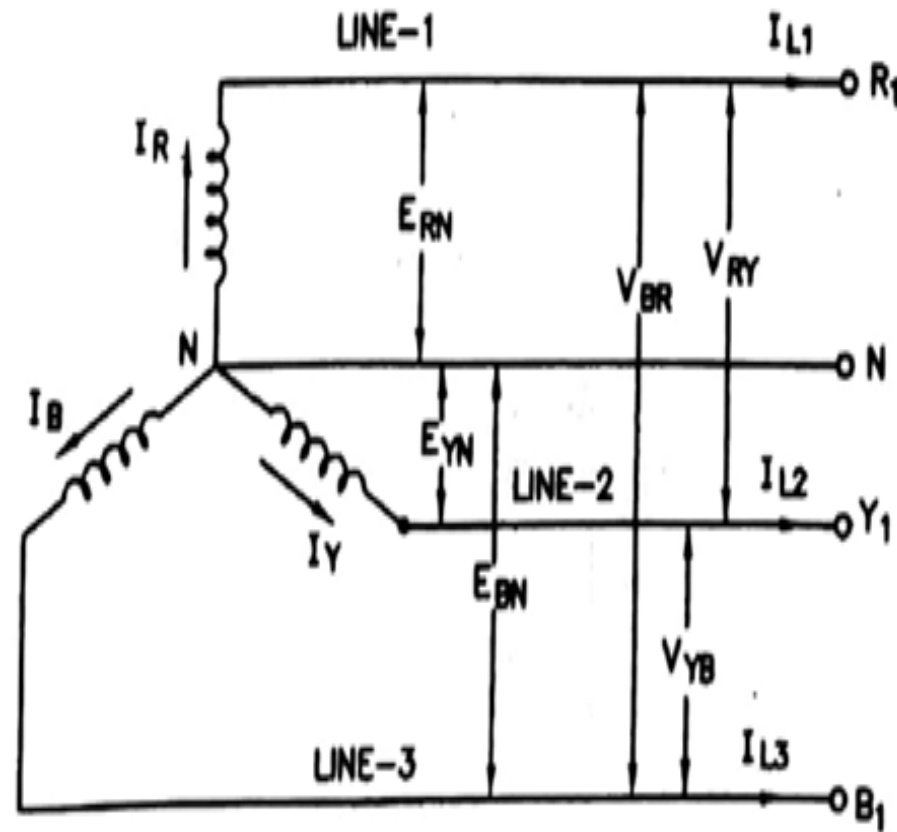
# Voltage and current relation in star connected system



- ▶ The emf across each winding is called phase voltage.
- ▶ They are denoted by  $E_{RN}$ ,  $E_{YN}$  and  $E_{BN}$ .
- ▶ The voltage between any two lines is called line voltage.
- ▶ They are represented by  $V_{RY}$ ,  $V_{YB}$  and  $V_{BR}$  respectively.
- ▶ Similarly currents flowing in the each winding is known as the phase current and current flowing in each line is called the line current.



- ▶ Since the system is balanced,  $I_R = I_Y = I_B = I_{Ph}$

$$I_{L1} = I_{L2} = I_{L3} = I_L$$

$$E_{RN} = E_{YN} = E_{BN} = E_{Ph}$$

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

- ▶ Relation between line current and phase current:

From Fig. 1, it is clear that

$$I_R = I_{L1} \rightarrow I_{Ph} = I_L$$

$$I_Y = I_{L2} \rightarrow I_{Ph} = I_L$$


$$I_B = I_{L3} \rightarrow I_{Ph} = I_L$$

Thus in star connection,

Line current, $I_L =$ Phase current, $I_{Ph}$
---



- ▶ **Relation between line voltage and phase voltage:**
- ▶ It is seen from figure that in star connection, there are two phase windings between each pair of line terminals.
- ▶ Since similar ends of these two winding are connected together, the emfs across them oppose each other and their instantaneous values will have opposite polarities.
- ▶ Therefore the rms value of line voltage between any two lines will be obtained by the vector difference of the two phase voltages.
- ▶ The phasor diagram of the phase emfs and currents in a star connected system is shown below:

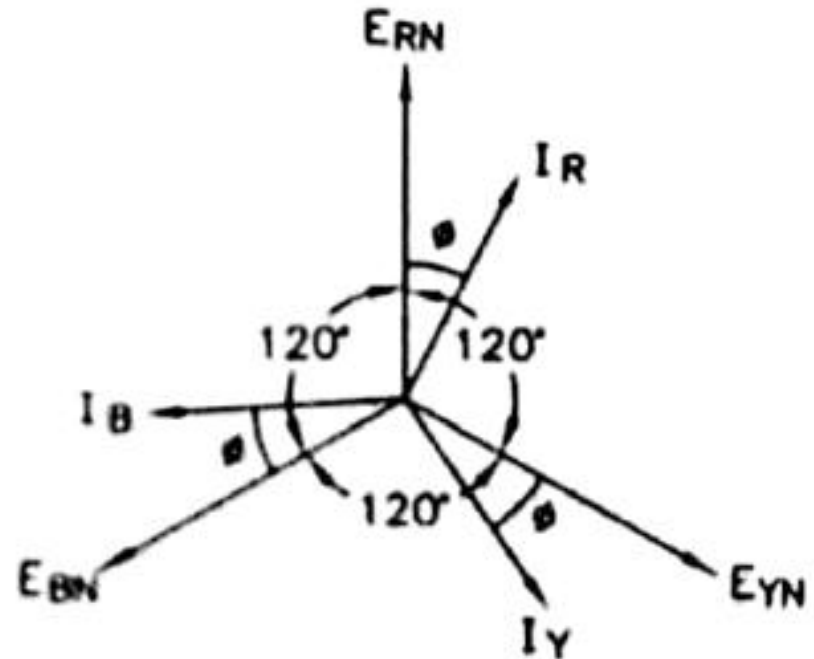


- Line voltage between terminals R and Y,  $V_{RY} = E_{RN} + E_{NY}$   
 $= E_{RN} + (-E_{YN})$   
 $= E_{RN} - E_{YN}$   
 $= \text{phasor difference}$

Similarly

$$E_{YB} = E_{YN} - E_{BN} \text{ and } E_{BR} = E_{BN} - E_{RN}$$

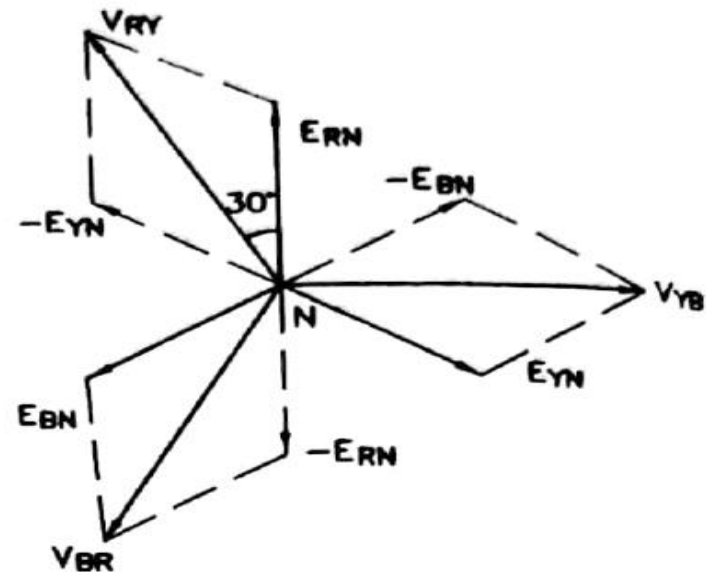- Hence it is clear that in a star connected system, the **line voltage** is obtained as the **vector difference** of the two corresponding phase voltages.
- This is shown in fig below, for examples  $V_{RY}$  is found by adding  $V_{RN}$  and  $V_{YN}$  reversed and its magnitude is given by the diagonal of the parallelogram.



- ▶ Since side of the parallelogram are of equal length and angle between two phase voltages is 60 degree.
- ▶ The line voltage is given by,

$$\begin{aligned} V_{RY} &= V_{RN} - V_{YN} \\ &= 2 V_{Ph} \cos \frac{60^\circ}{2} \\ &= 2 V_{Ph} \cos 30^\circ \\ &= 2 E_{Ph} \times \frac{\sqrt{3}}{2} \\ &= \sqrt{3} E_{Ph} \end{aligned}$$

Similarly  $V_{YB} = V_{BR} = \sqrt{3} E_{Ph} = V_L$

Thus in balanced star connected system,

$$V_L = \sqrt{3} E_{Ph}$$

i.e. Line voltage =  $\sqrt{3}$  × phase voltage

- The total power dissipated in the 3-phase star connected system is the arithmetic sum of the powers dissipated in the three phases.

$$\therefore \text{Total power} = 3 \times \text{power per phase}$$


$$= 3 \times V_{ph} \times I_{ph} \times \cos \phi$$

$$= 3 \times \frac{V_L}{\sqrt{3}} \times I_L \times \cos \phi$$

$$= \boxed{\sqrt{3} V_L I_L \cos \phi}$$

It should be noted that  $\phi$  is the angle between phase voltage and phase current and not between the line voltage and line current.
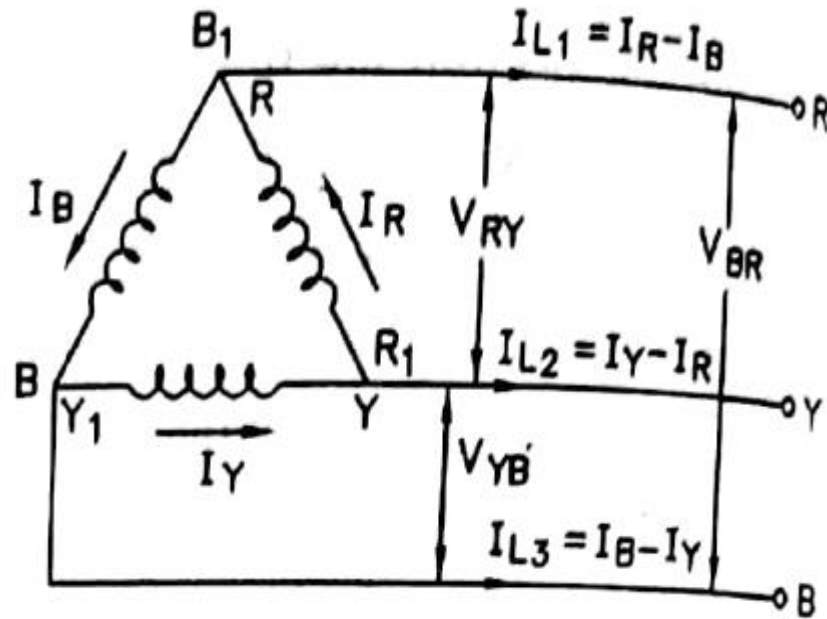
# Voltage and current relation in delta connected system



- ▶ The emf across each winding is called phase voltage.
- ▶ They are denoted by  $E_R$ ,  $E_Y$  and  $E_B$ .
- ▶ The voltage between any two lines is called line voltage.
- ▶ They are represented by  $V_{RY}$ ,  $V_{YB}$  and  $V_{BR}$  respectively.
- ▶ Similarly currents flowing in the each winding is known as the phase current and current flowing in each line is called the line current.

- ▶ Since the system is balanced,  $I_R = I_Y = I_B = I_{Ph}$   
 $I_{L1} = I_{L2} = I_{L3} = I_L$   
 $E_R = E_Y = E_B = E_{Ph}$   
 $V_{RY} = V_{YB} = V_{BR} = V_L$

- ▶ Relation between line voltage and phase voltage:

It is clear that

$$E_R = V_{RY} \rightarrow E_{Ph} = V_L$$

$$E_Y = V_{YB} \rightarrow E_{Ph} = V_L$$


$$E_B = V_{BR} \rightarrow E_{Ph} = V_L$$

Thus in delta connection,

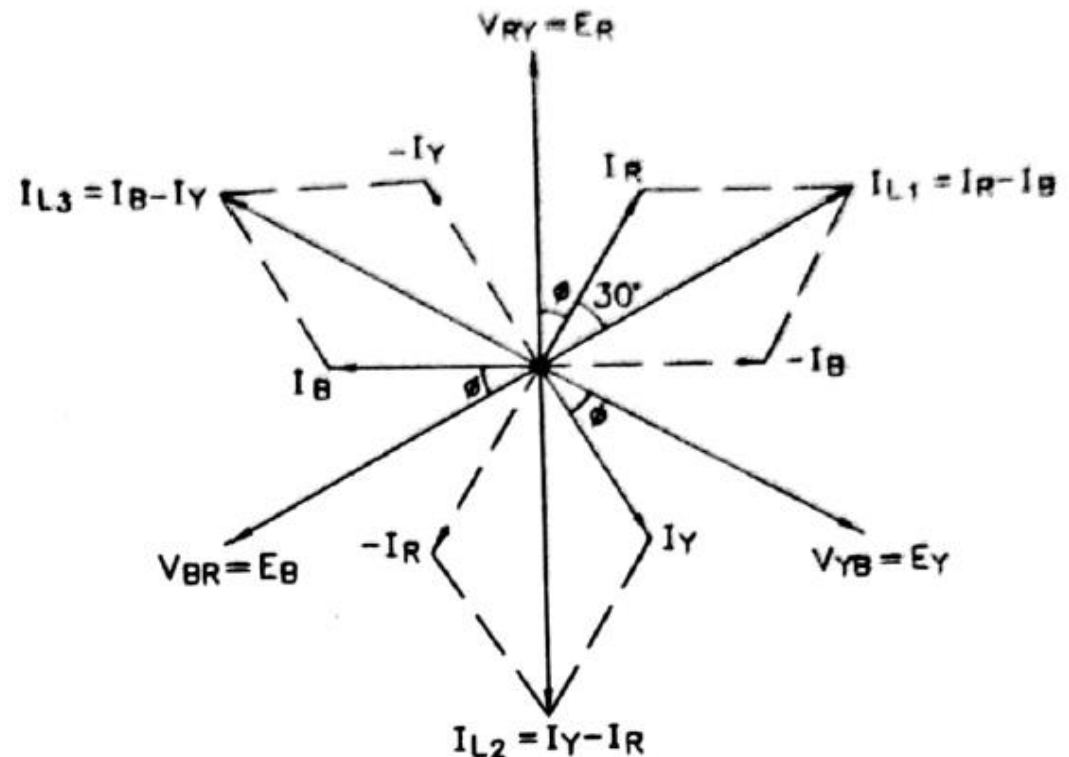**Line voltage,  $V_L$  = Phase voltage,  $E_{Ph}$**

► **Relation between line current and phase current:**

- It is seen from figure that current flowing in each line is the vector difference of the two phase currents.
- Current in line 1,  $I_{L1} = I_R - I_B$
- Current in line 2,  $I_{L2} = I_Y - I_R$
- Current in line 3,  $I_{L3} = I_B - I_Y$
- Current in line 1 can be found as the vector difference of the two corresponding phase currents. This is shown in figure below:





- ▶  $I_{L1}$  can be obtained by adding  $I_R$  and  $I_B$  reversed and its value is given by the diagonal of the parallelogram as shown in vector diagram.
- ▶ Since the sides of parallelogram are equal in magnitude and the angle between them is 60 degree, the line current is given as:

$$I_{L1} = I_R - I_B \text{ (vector difference)}$$

$$= 2 \times I_{Ph} \times \cos \frac{60^\circ}{2}$$

$$= 2 \times I_{Ph} \times \cos 30^\circ$$

$$= 2 \times I_{Ph} \times \frac{\sqrt{3}}{2}$$

$$= \sqrt{3} I_{Ph}$$

$$\text{Similarly } I_{L2} = I_{L3} = \sqrt{3} I_{Ph} = I_L$$

Thus, in delta connection,

$$\text{Line current, } I_L = \sqrt{3} \times \text{Phase current}$$

- ▶ The total power in the 3-phase circuit is equal to the arithmetic sum of three phase power.
- ▶ Hence,

Total power =  $3 \times$  power per phase

$$= 3 \times V_{ph} I_{ph} \cos \phi$$

1. A 415 V, 3-phase voltage is applied to a balanced star-connected 3-phase load of phase impedance  $(3+j4)$  ohms each. Calculate (i) line current and (ii) total power supplied in kW.

Solution:- star connection  $V_L = 415 \text{ V}$

$$Z_{ph} = 3 + j 4$$

$$V_p = \frac{V_L}{\sqrt{3}}$$

$$Z_{ph} = 3 + j 4$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}}$$

$$= \frac{415}{\sqrt{3}}$$

$$= \sqrt{3^2 + 4^2}$$

$$= \frac{239.6}{5}$$

$$= 239.6 \text{ Volt}$$

$$= 5 \Omega$$

$$= 47.92 \text{ A}$$

$$\therefore I_L = I_{ph} = \boxed{47.92 \text{ A}}$$

$$\cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{3}{5} = 0.6$$

$$\text{Power} = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 415 \times 47.92 \times 0.6$$

$$= \boxed{20.666 \text{ kW}}$$

2. A balanced mesh-connected load of  $6+j8$  ohms per phase is connected to a 3-phase, 230 V supply. Find the line current, p.f and power.

Solution:- Connection Delta

$$Z_{ph} = 6 + j 8$$

$$= 10 \Omega \text{ (magnitude)}$$

$$V_L = V_{ph} = 230 \text{ V}$$

$$\therefore I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230}{10} = 23 \text{ A}$$

$$\therefore I_L = \sqrt{3} I_{ph} = \sqrt{3} \times 23 = \boxed{39.83 \text{ A}}$$

$$\text{Power factor} = \cos \phi = \frac{R_{ph}}{Z_{ph}}$$

$$= \frac{6}{10}$$

$$= \boxed{0.6 \text{ (lag)}}$$

$$\text{Power} = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 230 \times 39.83 \times 0.6$$

$$= \boxed{9.520 \text{ kW}}$$

3. Three similar coils each of resistance 15 ohms and inductance of 0.25 H are connected (i) in star and (ii) in delta to a 3-phase, 400 V, 50 Hz supply. Calculate line and phase values of current and voltage in both the cases. Also calculate the power absorbed.

Solution:-  $R_{ph} = 15 \Omega$  ,  $L_{ph} = 0.25 \text{ H}$      $X_{ph} = \omega L_{ph} = 2 \times \pi \times 50 \times 0.25 = 78.54$

$$Z_{ph} = \sqrt{R_{ph}^2 + X_{ph}^2} = \sqrt{15^2 + 78.54^2} = 79.96 \Omega$$

**Star connection :**

$$V_L = \boxed{400 \text{ V}}$$

$$\text{Power factor } \cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{15}{79.96} = \boxed{0.1875 \text{ (lagging)}}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = \boxed{230.94 \text{ V}}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{79.96} = \boxed{2.888 \text{ A}}$$

$$I_L = I_{ph} = \boxed{2.888 \text{ A}}$$

$$\begin{aligned} \text{Total power} &= \sqrt{3} V_L I_L \cos \phi \quad (\text{or} = 3 \times V_{ph} \times I_{ph} \cos \phi) \\ &= \sqrt{3} \times 400 \times 2.888 \times 0.1875 \\ &= \boxed{375.17 \text{ W}} \end{aligned}$$

**Delta connection :**

$$V_L = \boxed{400 \text{ V}}$$

$$V_{Ph} = V_L = \boxed{400 \text{ V}}$$

$$I_{Ph} = \frac{V_{Ph}}{Z_{Ph}} = \frac{400}{79.96} = \boxed{5.0025 \text{ A}}$$

$$I_L = \sqrt{3} I_{Ph} = \sqrt{3} \times 5.0025 = \boxed{8.664 \text{ A}}$$

$$\cos \phi = \frac{R_{Ph}}{Z_{Ph}} = \frac{15}{79.96} = \boxed{0.1875 \text{ (lag)}}$$

$$\begin{aligned} \text{Total power} &= \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 400 \times 8.664 \times 0.1875 \\ &= \boxed{1125.56 \text{ watt}} \end{aligned}$$

Thank you!